



Ain Shams University

Faculty of Engineering

Postgraduate Program
(Master in Computer and Systems Engineering)

CSE620: Advanced Computer Architecture

Bonus Assignment

HDL Testbench

Register File

Elaborated By:

Eng. Youssef Nasser

2300315

Supervised by:

Prof. Mohamed Watheq Ali Kamel El-Kharashi

Contents

List of Figures	3
List of Tables.....	3
Register File Problem Statement	4
Circuit Diagram	4
RTL Code	5
Test Strategy.....	8
Testbench.....	9
Linux Environment	15
Makefile.....	16
Simulation Results	17
Simulation Tools	19

List of Figures

Figure 1 Dummy Register File	4
Figure 2 Circuit Diagram for Dual-Port Register File	4
Figure 3 Verdi Console	17
Figure 4 Verdi Environment	18
Figure 5 Verdi Content Memory	18

List of Tables

Table 1 Test Strategy	8
-----------------------------	---

Register File Problem Statement

Using VHDL or Verilog model a register file that contains 2^n 32-bit registers. The register file has two read port and two write ports. Below is a symbol of this register file, showing all input and output signals with their bit-widths.

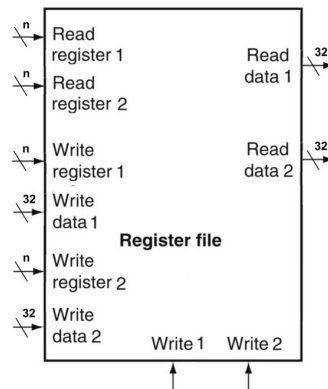


Figure 1 Dummy Register File

Circuit Diagram

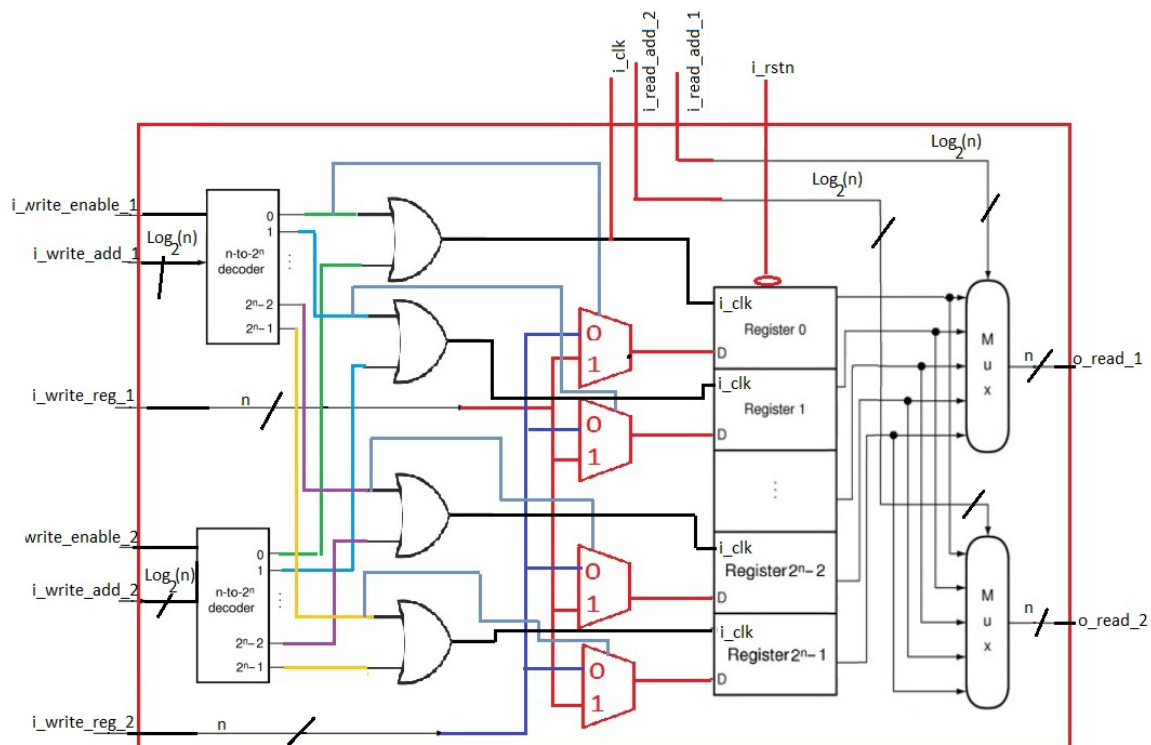


Figure 2 Circuit Diagram for Dual-Port Register File

If the two writing ports writes at the same address it will be written at port 1 by using Priority encoder.

RTL Code

```

/*****
* Master Advanced Computer Architecture Course CSE620
*
* Module: Dual Port Register File
*
* Description:
* This Verilog module implements a simple dual-port register file with
* Asynchronous reset functionality. It allows simultaneous read and write
* Operations on two ports. The register file is parameterized with data width
* And address depth.
*
* Parameters:
* - data_width: Width of each register in bits (default: 32)
* - Address_depth: Number of registers in the file (default: 4)
*
* Ports:
* - i_clk: Clock input for synchronous operations
* - i_rstn: Active-low asynchronous reset input
*
* Write Port 1:
* - i_write_enable_1: Write enable signal for port 1
* - i_write_reg_1: Data input for write port 1
* - i_write_add_1: Address input for write port 1
*
* Write Port 2:
* - i_write_enable_2: Write enable signal for port 2
* - i_write_reg_2: Data input for write port 2
* - i_write_add_2: Address input for write port 2
*
* Read Port 1:
* - i_read_add_1: Address input for read port 1
* - o_read_1: Data output for read port 1
*
* Read Port 2:
* - i_read_add_2: Address input for read port 2
* - o_read_2: Data output for read port 2
*
* Memory Organization:
* - The register file is implemented as an array named Dual_RF with data_width
*   Bits for each register and 2^Address_depth registers.
*
* Reset Behavior:
* - Upon assertion of the asynchronous reset (i_rstn), all registers are
*   Cleared to 0.
*
* Write Operation:
* - If both write ports are enabled simultaneously and have the same address,
*   The data from write port 1 is written to the specified address.
* - If only one write port is enabled, data is written to the specified address
*   For that port.
*
* Read Operation:
* - Data is read from the specified address for each read port independently.
*
* Student Name: Youssef Nasser
* Student ID: 2300315
* Date: 12/12/2023
* Issued for: Master Final Project (Bonus)
*****/

```

```

// Specify the timescale for simulation, with 1ns time units and 1ps
precision
`timescale 1ns/1ps
module regfile #(parameter data_width = 32 , Address_depth = 4) (
    input wire i_clk,        // Clock input
    input wire i_rstn,       // write port 1
    // Write port 1 inputs
    input wire i_write_enable_1,
    input wire [data_width-1:0] i_write_reg_1,
    input wire [Address_depth-1:0] i_write_add_1,
    //write port 2
    input wire i_write_enable_2,
    input wire [data_width-1:0] i_write_reg_2,
    input wire [Address_depth-1:0] i_write_add_2,
    // read port 1
    input wire [Address_depth-1:0] i_read_add_1,
    output wire [data_width-1:0] o_read_1,
    // read port 2
    input wire [Address_depth-1:0] i_read_add_2,
    output wire [data_width-1:0] o_read_2
);

    // Declare an array Dual_RF as a memory with specified data_width and
    Address_depth
    reg [data_width-1:0] Dual_RF [0:((2**Address_depth)-1)]; // 0:15

    // Declare an integer variable i for loop indexing
    integer i;

    // Always block triggered by the positive edge of the clock or negative
    edge of the asynchronous reset
    always@(posedge i_clk or negedge i_rstn) begin
        if (!i_rstn) begin
            // Reset condition: set all memory locations to 0
            for(i=0;i<(2**Address_depth);i=i+1)
                begin
                    Dual_RF[i] <= 0;
                end
        end
    end

```

```
else
    begin
        // Write Operation
        // handling the case when both write ports try to write to the same
        register
        if(i_write_enable_1 && i_write_enable_2 && (i_write_add_1 ==
i_write_add_2) )
            begin
                Dual_RF[i_write_add_1] <= i_write_reg_1;
            end

        else
            begin
                if (i_write_enable_1)
                    Dual_RF[i_write_add_1] <= i_write_reg_1;

                if (i_write_enable_2)
                    Dual_RF[i_write_add_2] <= i_write_reg_2;

            end

        end

    end

    // Assign read outputs based on read addresses
    assign o_read_1 = Dual_RF[i_read_add_1];
    assign o_read_2 = Dual_RF[i_read_add_2];
endmodule
```

Test Strategy

Reset pin

i_rstn

Write Port 1 Pins

i_write_enable_1 , i_write_reg_1 , i_write_add_1

Write Port 2 Pins

i_write_enable_2 , i_write_reg_2 , i_write_add_2

Read Port 1 Pin

i_read_add_1

Read Port 2 Pin

i_read_add_2

First, we need to initialize inputs , then reset sequence and waiting a delta cycle to avoid metastability then running the following test vectors.

For initialization there is a task for it at the testbench code , reset sequence has a task too and the delta cycle is clock period / 10 .

Clock Frequency is 20 ns which is $1000/20 \rightarrow 50$ MHz

Table 1 Test Strategy

Test ID	Test Feature	Inputs	Delay	Expected Output
1	Write and read interaction at port 1	Reset is 1 Write Port 1 is on Adds 0 , Data 10 Read address 1,2 are 0	44 ns	Read Port 1 -> 10 Read Port 1 -> 10
2	Write and read interaction at port 2	Reset is 1 Write Port 2 is on Adds 15 , Data 9 Read address 1,2 are 15	44 ns	Read Port 1 -> 9 Read Port 1 -> 9
3	Simultaneous Writes and Reads	Reset is 1 Write port 1 , 2 are on Adds1 is 4 and Adds 2 is 5 Data is 7 , 8 Read address 1,2 are 4 , 5	44 ns	Read Port 1 -> 7 Read Port 1 -> 8
4	Overlapping Writes and reads	Reset is 1 Write port 1 , 2 are on Adds1 and Adds 2 are 10 Data is 22 , 33 Read address 1,2 are 10	44 ns	Read Port 1 -> 22 Read Port 1 -> 22

Testbench

```

/*****
* Testbench: regfile_tb
*
* Description:
* This Verilog testbench is designed to verify the functionality of the
* regfile module. It includes test cases to perform write and read operations
* on the dual-port register file and checks the output against expected values.
*
* Parameters:
* - clk_period: Clock period (default: 20 time units)
* - data_width: Width of each register in bits (default: 32)
* - Address_depth: Number of registers in the file (default: 4)
* - delta_cycle: Time delay for simulation purposes (default: clk_period/10)
*
* Testbench Ports:
* - i_clk: Clock input for synchronous operations
* - i_rstn: Active-low asynchronous reset input
* - Various input and output ports for the regfile module
*
* Tasks:
* - initialization: Sets initial values for testbench variables
* - reset_sequence: Performs a reset sequence on the regfile module
* - write_operation: Simulates a write operation on a specified port
* - read_scoreboard: Checks the output of a read operation against expected data
* - clear: Resets all testbench variables
* - clock_cycle: Advances the simulation time by one clock cycle
*
* Simulation Flow:
* 1. Initialization of variables
* 2. Reset sequence to initialize the regfile module
* 3. Test Case 1: Write data to port 1, perform read operations, and check results
* 4. Test Case 2: Write data to port 2, perform read operations, and check results
* 5. Test Case 3: Simultaneous writes to both ports, read operations, and checks
* 6. Test Case 4: Overlapping writes on the same address, read operations, and checks
* 7. End of simulations after a certain number of clock cycles
*
* Student Name: Youssef Nasser
* Student ID: 2300315
* Date: 12/12/2023
*****/

// Begin regfile_tb module
module regfile_tb;

// Parameters
localparam clk_period    = 20;
localparam data_width    = 32;
localparam Address_depth = 4;
localparam delta_cycle = (clk_period/10);

// TB ports
reg i_clk;
reg i_rstn;
// Write port 1
reg i_write_enable_1;
reg [data_width-1:0] i_write_reg_1;
reg [Address_depth-1:0] i_write_add_1;
// Write port 2
reg i_write_enable_2;
reg [data_width-1:0] i_write_reg_2;
reg [Address_depth-1:0] i_write_add_2;
// Read port 1
reg [Address_depth-1:0] i_read_add_1;
wire [data_width-1:0] o_read_1;
// Read port 2
reg [Address_depth-1:0] i_read_add_2;
wire [data_width-1:0] o_read_2;

```

```

/*****
 * Instantiate regfile module
 *****/
regfile #(data_width, Address_depth) CUT (
    .i_clk(i_clk),
    .i_rstn(i_rstn),
    // Write port 1
    .i_write_enable_1(i_write_enable_1),
    .i_write_reg_1(i_write_reg_1),
    .i_write_add_1(i_write_add_1),
    // Write port 2
    .i_write_enable_2(i_write_enable_2),
    .i_write_reg_2(i_write_reg_2),
    .i_write_add_2(i_write_add_2),
    // Read port 1
    .i_read_add_1(i_read_add_1),
    .o_read_1(o_read_1),
    // Read port 2
    .i_read_add_2(i_read_add_2),
    .o_read_2(o_read_2)
);

/*****
 * Task to initialize testbench variables
 *****/
task initialization;
begin
    $display("Initialization start at time %0t", $time);
    i_write_enable_1 = 0;
    i_write_reg_1 = 0;
    i_write_add_1 = 0;
    i_write_enable_2 = 0;
    i_write_reg_2 = 0;
    i_write_add_2 = 0;
    i_read_add_1 = 0;
    i_read_add_2 = 0;
end
endtask

```

```

/*****
 * Task to perform a reset sequence
 *****/
task reset_sequence;
begin
    i_rstn = 0;
    $display("Reset is active low, reset now is %0d at time %0t", i_rstn,
$time);
    #(clk_period*10);
    i_rstn = 1;
end
endtask

/*****
 * Task to simulate a write operation on a specified port
 *****/
task write_operation;
input reg [1:0] ID;
input reg [Address_depth-1:0] adds;
input reg [data_width-1:0] data;
begin
    $display("Write operation from port %0d at time %0t", ID, $time);
    $display("Address is %0d, data in is %0d", adds, data);
    case (ID)
        1: begin
            i_write_enable_1 = 1;
            i_write_reg_1 = data;
            i_write_add_1 = adds;
        end
        2: begin
            i_write_enable_2 = 1;
            i_write_reg_2 = data;
            i_write_add_2 = adds;
        end
        default: begin
            $display("Invalid ID");
        end
    endcase
end
endtask

```

```

/*****
 * Task to check the output of a read operation against expected data
 *****/
task read_scoreboard;
input reg [1:0] ID;
input reg [Address_depth-1:0] adds;
input reg [data_width-1:0] expected_data;
begin
    $display("Read check operation from port %0d at time %0t", ID, $time);
    $display("Address is %0d, expected data is %0d", adds, expected_data);
    case (ID)
        1: begin
            i_read_add_1 = adds;
            #delta_cycle;
            if (o_read_1 == expected_data) begin
                $display("Read Test passed");
            end else begin
                $display("Read test failed");
            end
        end
        2: begin
            i_read_add_2 = adds;
            #delta_cycle;
            if (o_read_2 == expected_data) begin
                $display("Read Test passed");
            end else begin
                $display("Read test failed");
            end
        end
        default: begin
            $display("Invalid ID");
        end
    endcase
end
endtask

/*****
 * Task to clear all testbench variables
 *****/
task clear;
begin
    i_write_enable_1 = 0;
    i_write_reg_1 = 0;
    i_write_add_1 = 0;
    i_write_enable_2 = 0;
    i_write_reg_2 = 0;
    i_write_add_2 = 0;
    i_read_add_1 = 0;
    i_read_add_2 = 0;
end
endtask

```

```

/*****
 * Task to advance simulation time by one clock cycle
 *****/
task clock_cycle;
begin
    #clk_period;
end
endtask

/*****
 * Initial block for clock generation
 *****/
initial begin
    i_clk = 0;
    forever begin
        #(clk_period/2) i_clk = ~i_clk;
    end
end

/*****
 * Initial block for simulation setup
 *****/
initial begin
    // Dumping waveform to a VCD file
    $dumpfile("regfile.vcd");
    $dumpvars(0, regfile_tb);

    // Dumping FSDB File (Fast Signal Database) needed for Verdi

    $fsdbDumpfile("tb.fsdb");
    $fsdbDumpvars;

    $display("Welcome to testbench");

    // Execute test cases
    initialization;
    reset_sequence;
    #delta_cycle;

    // Test Case 1
    $display("Test Case 1");
    write_operation(1, 0, 10);
    clock_cycle;
    clear;
    read_scoreboard(1, 0, 10);
    read_scoreboard(2, 0, 10);
    clock_cycle;

    // Test Case 2
    $display("Test Case 2");
    write_operation(2, 15, 9);
    clock_cycle;
    clear;
    read_scoreboard(1, 15, 9);
    read_scoreboard(2, 15, 9);
    clock_cycle;

```

```
// Test Case 3
$display("Test Case 3");
write_operation(1, 4, 7);
write_operation(2, 5, 8);
clock_cycle;
clear;
read_scoreboard(1, 4, 7);
read_scoreboard(2, 5, 8);
clock_cycle;

// Test Case 4
$display("Test Case 4");
write_operation(1, 10, 22);
write_operation(2, 10, 33);
clock_cycle;
clear;
read_scoreboard(1, 10, 22);
read_scoreboard(2, 10, 22);

// End of simulations
#(clk_period*100);
$display("End of Simulations");
$finish;
end
endmodule
```

Linux Environment

rtl.f has the following two lines

```
./regfile.v
```

```
./regfile_tb.v
```

Make directory that has the following files:

```
Makefile
```

```
regfile_tb.v
```

```
regfile.v
```

```
rtl.f
```

```
make comp
```

Makefile

```

#-----
# comp: Target that invokes the clean, vcs, and verdi targets in sequence.
#-----

comp : clean vcs verdi
#-----
# vcs: Target to compile the Verilog source files using Synopsys VCS
#simulator.
# Options:
# -f rtl.f : Specifies the file containing the list of #
# Verilog source files.
# -cm line+fsm+tgl+branch+cond : Enable code coverage metrics (line,
FSM, toggle, branch, condition).
# -timescale=1ns/1ps : Sets the timescale for simulation.
# +vcs+flush+all : Enable flushing of files after simulation.
# -full64 : Enables 64-bit compilation.
# -R : Runs the simulation.
# +vc : Enables Verilog Compiler mode.
# +v2k : Enables Verilog-2001 features.
# -fsdb : Generates FSDB (Full Signal Database) file for debugging.
# -debug_all : Enables debugging for all modules.
# -l run.log : Redirects log output to run.log.
#-----
vcs :
    vcs -f rtl.f -cm line+fsm+tgl+branch+cond -timescale=1ns/1ps
+vcs+flush+all -full64 -R +vc +v2k -fsdb -debug_all -l run.log
#-----
# verdi: Target to launch the Synopsys Verdi debugger with the specified
options.
# Options:
# -f rtl.f : Specifies the file containing the list of Verilog
source files.
# -ssf tb.fsdb : Specifies the FSDB file to load into Verdi.
# & : Runs Verdi in the background.
#-----
verdi :
    verdi -f rtl.f -ssf tb.fsdb &
#-----
# clean: Target to remove generated files and clean the working directory.
#-----

clean :
    rm -rf *~ core csrc simv* group_2* vc_hdrs.h ucli.key urg*
*.log novas.* *.fsdb* verdiLog 64* DVEfiles *.vpd group_2.daidir
group_2.vdb wave.vcd
#-----

```


Simulation Results

```
12 Verdi>run
13 *Verdi* : Begin traversing the scopes, layer (0).
14 *Verdi* : End of traversing.
15 Welcome to testbench
16 Initialization start at time 0
17 Reset is active low, reset now is 0 at time 0
18 Test Case 1
19 Write operation from port 1 at time 202000
20 Address is 0, data in is 10
21 Read check operation from port 1 at time 222000
22 Address is 0, expected data is 10
23 Read Test passed
24 Read check operation from port 2 at time 224000
25 Address is 0, expected data is 10
26 Read Test passed
27 Test Case 2
28 Write operation from port 2 at time 246000
29 Address is 15, data in is 9
30 Read check operation from port 1 at time 266000
31 Address is 15, expected data is 9
32 Read Test passed
33 Read check operation from port 2 at time 268000
34 Address is 15, expected data is 9
35 Read Test passed
36 Test Case 3
37 Write operation from port 1 at time 290000
38 Address is 4, data in is 7
39 Write operation from port 2 at time 290000
40 Address is 5, data in is 8
41 Read check operation from port 1 at time 310000
42 Address is 4, expected data is 7
43 Read Test passed
44 Read check operation from port 2 at time 312000
45 Address is 5, expected data is 8
46 Read Test passed
47 Test Case 4
48 Write operation from port 1 at time 334000
49 Address is 10, data in is 22
50 Write operation from port 2 at time 334000
51 Address is 10, data in is 33
52 Read check operation from port 1 at time 354000
53 Address is 10, expected data is 22
54 Read Test passed
55 Read check operation from port 2 at time 356000
56 Address is 10, expected data is 22
57 Read Test passed
58 End of Simulations
59 $finish called from file "./regfile_tb.v", line 278.
60 $finish at simulation time 2358000
61 Simulation complete, time is 2358000 ps.
```

Figure 3 Verdi Console

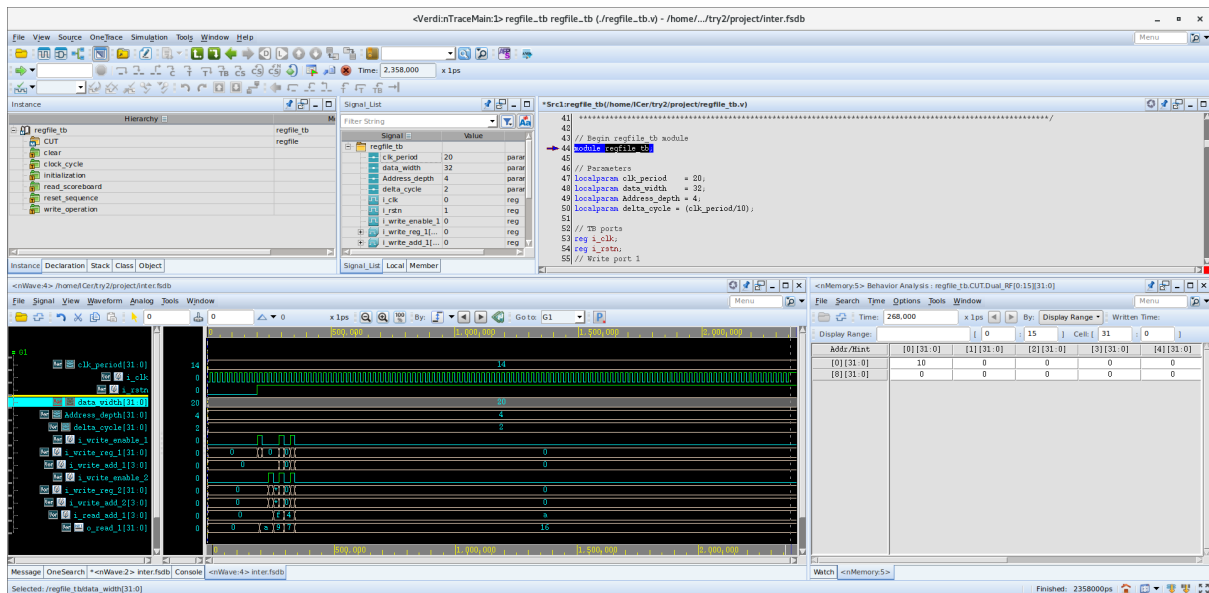


Figure 4 Verdi Environment

 


Figure 5 Verdi Content Memory

Test Case 1 data at address 0 is 10.

Test Case 2 data at address 15 is 9

Test Case 3 data at address 4 is 7, data at address 5 is 8

Test Case 4 data at address 10 is 22 how ever both 2 ports are writing at the same address by the priority of port1

Simulation Tools

1. **gedit:**

Text editor for writing code. It is a lightweight and simple editor commonly used on Linux systems.

2. **GNU Make:**

The native implementation of the Make utility on Linux. It interprets Makefiles to manage the build process of software projects.

3. **VCS:**

Synopsys VCS (Verilog Compiler Simulator) is a high-performance simulator for digital designs. It's commonly used in the hardware verification domain.

4. **Verdi:**

Synopsys Verdi is a debug and visualization tool for hardware designs. It helps in the verification and debugging process, providing features like waveform viewing, transaction-level debugging, and more.